




Maulana Azad National Institute Of Technology,

Assignment - 3 Bhopal

Roll No. Scholar No.


Name - Vivek Singh Kanwar
Scholar number - 211113025

Branch : Electrical
Section : I

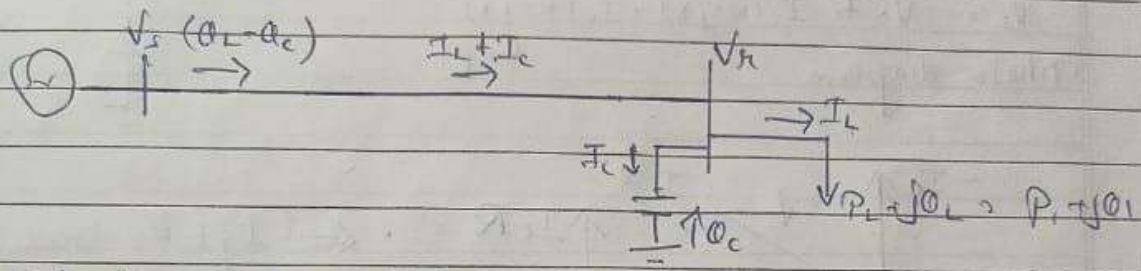

Initially, without shunt capacitor
current draw I_L lags V_R
after shunt capacitor,
capacitor takes leading current I_C

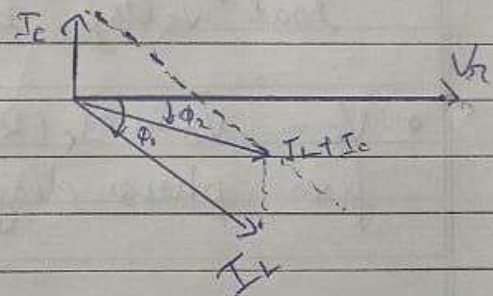Initial pf angle ϕ_1
after shunt capacitor
pf angle = ϕ_2
 $\phi_1 > \phi_2$
 $\cos \phi_1 < \cos \phi_2$
 $\text{pf}_1 < \text{pf}_2$



hence power factor improved

$$\text{Voltage drop} = |V_s| - |V_R|$$

$$= IR \cos \phi + IX \sin \phi$$

if R neglected as compare to X
 $IR \cos \phi \approx 0$



$$\text{then voltage drop} = IX \sin \phi$$

after shunt capacitance $\phi \downarrow \Rightarrow \sin \phi \downarrow$
hence voltage drop $|V_s| - |V_R|$ reduces
and voltage regulation improved

2) Under lightly load condition $I_L = 0$ (load current only I_c is drawn under normal condition)

$$V_s = V_r + I_c(R+jX) + I_c(R+jX)$$

Phase diagram

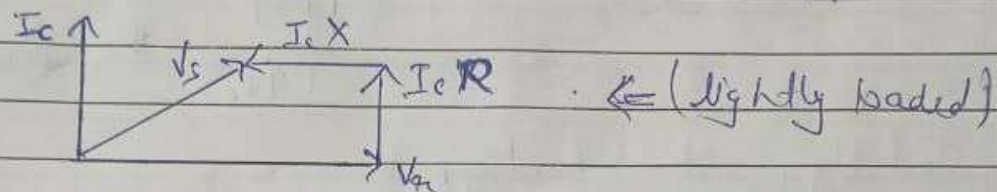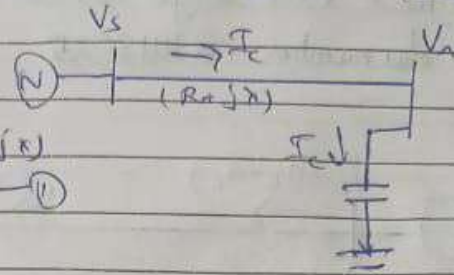


Under lightly loaded condition load voltage is increased load voltage becomes more than source voltage


$$V_s = V_r + I_c(R+jX) \quad (2)$$

from phasor diagram we can see $V_r > V_s$

3) ~~Before~~ Before Series capacitance

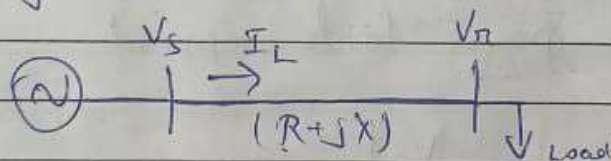

$$V_s = V_r + I_L(R+jX)$$

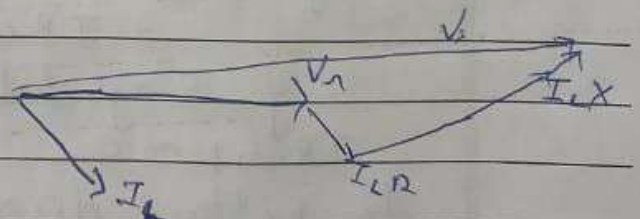




MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY,
BHOPAL


Roll No.

Scholar No.

After series capacitor added

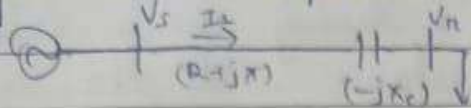

$$V_s = V_n + I_L (R + jX - jX_c)$$

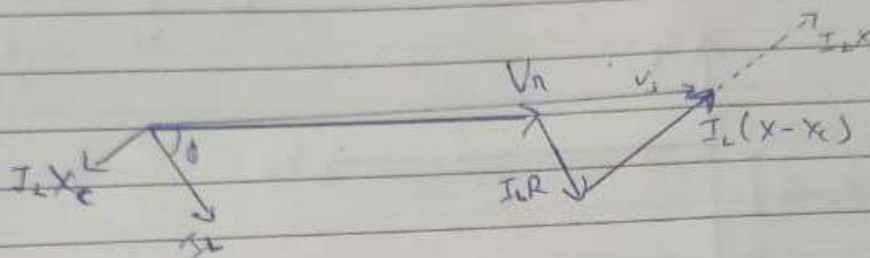

→ Hence line reactance is reduced

Voltage drop before series compensation

$$|V_s| - |V_n| = I R \cos \phi + I X \sin \phi$$

neglecting R as very small in line. ($R \ll X$)



$$|V_s| - |V_n| = I X \sin \phi \quad \text{--- (1)}$$

Voltage drop after series compensation (capacitor)

$$|V_s| - |V_n| = I (X - X_c) \sin \phi \quad \text{--- (2)}$$

from (1) and (2) we can say voltage drop reduces after adding series compensation capacitor and hence voltage regulation is improved

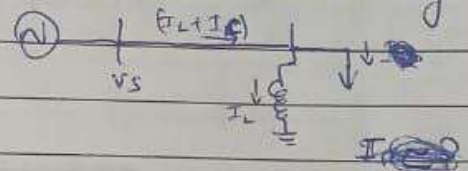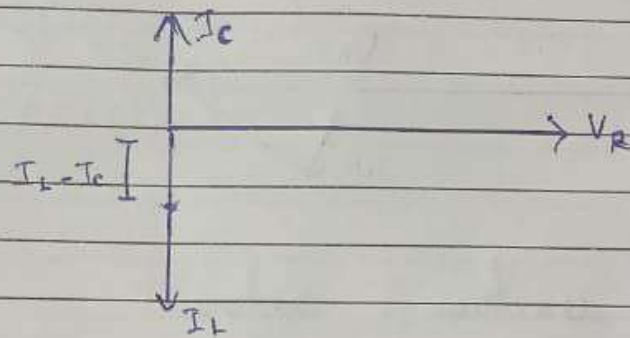4) In lightly loading condition only line charging current (I_c) flows ($I_L \approx 0$), so a leading power factor is there. After adding shunt inductance, the inductor draws lagging current thus controlling power factor.



Adding shunt inductor draws a lagging current reducing phase angle b/w V and net current I . This helps in improving power factor and reduce reactive power demand.

5) Use of Series inductor compensation system in power system


- Series inductor can be used to compensate for excessive line capacitance especially in long transmission line.
- Series inductor introduces a voltage drop V_T that partially cancels the voltage drop across the line capacitance.
- This reduces the overall voltage drop across the line improving voltage regulation.



**Maulana Azad National Institute Of Technology,
Bhopal**

Roll No. Scholar No.

(i) DC excitation system

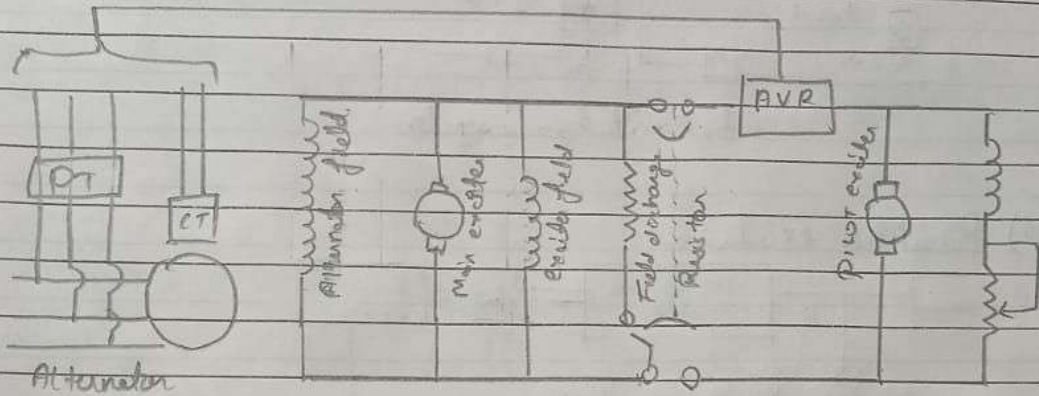


- The DC excitation system includes two exciters, the main exciter and pilot exciter
- Exciter drive. Both exciters can be driven by the main shaft or by a separate motor
Shaft driven exciters are preferred as they maintain unit-system operation and less affected by external disturbances
- Automatic voltage Regulator:- Adjust exciter o/p to control alternator terminal voltage
- field discharge Resistor:- engages when field breaker is open to dissipate energy stored in inductive field winding

(ii) Static excitation system:-


In this method the excitation power for main alternator field is drawn from o/p terminal of main 3 ϕ alternator. This 3 ϕ voltage is fed to 3 ϕ full converter bridge using thyristor. The firing angle of thyristor controlled by means of regulator which picks up signal from alternator terminal through PT. The controlled power ^{power} _{and} delivered to field wind of main alternator through brushes and slip rings.

ADTAB

Roll No. Scholar No.

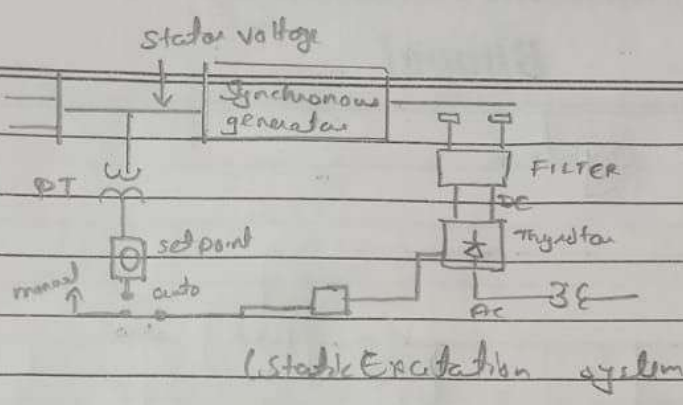

(ii) Brushless excitation

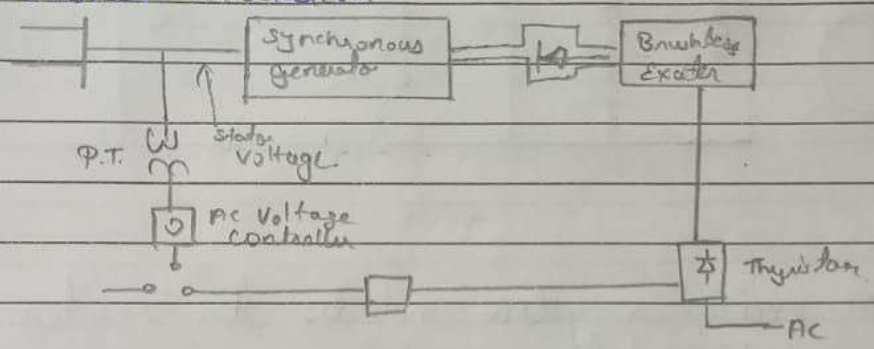

In this the exciter is actually small ac generator built on end of gen. shaft instead of rings, in this exciter a stationary mag. field is provided from DC winding which is wound on stator. The rotor winding produces ac voltage and this is fed directly into diode type rectifier which are built into the shaft/shaft so as to have in effect a rotating rectifier. The DC o/p from rectifier is connected directly to main rotor ~~ac~~ winding through leads which pass inside shaft. There is no need for collector rings or brushes. The thyristor DC o/p is controlled by controlling the firing angle which is governed by field voltage regulator.